

1. Identify Basic Steps:

- Load A into R1.
- Load B into R2.
- Square the value in R1.
- Multiply the squared value in R1 with A.
- Multiply the value in R2 with B.
- Add the results of the previous two operations.
- Add C to the result.
- Output the final result.

2. Sequence of Steps:

- Step 0: Load A into R1.
- Step 1: Load B into R2.
- Step 2: Square the value in R1.
- Step 3: Multiply the squared value in R1 with A.
- Step 4: Multiply the value in R2 with B.
- Step 5: Add the results of steps 3 and 4.
- Step 6: Add C to the result.
- Step 7: Output the final result and set Done=1.

3. Create Table:

4. Truth Table:

5. Number of Flip-flops:

From the truth table, we observe that we need at least 3 flip-flops to represent the states. These flip-flops will be used to store the current step, ensuring the FSM progresses through the correct sequence of steps.

This design ensures the computation is performed efficiently with the minimum number of steps and flip-flops required.

[illegible]

Step	Operation	R1	R2	Control Signals	Next Step
0	Load A into R1	A	-	Load R1, Mux1: A	1
1	Load B into R2	A	B	Load R2, Mux2: B	2
2	Square the value in R1	A2A2	B	ALU: Square, Mux1: R1	3
3	Multiply R1 with A	A2A2	AB	ALU: Multiply, Mux1: R1, Mux2: A	4
4	Multiply R2 with B	A2A2	B2B2	ALU: Multiply, Mux1: R2, Mux2: B	5
5	Add results of steps 3 & 4	A2A2	B2B2	ALU: Add, Mux1: R1, Mux2: R2	6
6	Add C to the result	A2A2	B2B2	ALU: Add, Mux1: R1, Mux2: C	7
7	Output the result	A2A2	B2B2	Output, Done=1	-